

# **IBM ASSIGNMENT- I**

**TEAM ID : PNT2022TMID2663**


**NAME : BALAMURUGAN U**

**ROLL NO : 212919106014**

Create a circuit with Piezo alarm, PIR Sensor, TMP Sensor with below functionalities:

- 1.Alarm should sound in one manner if temp is above 60C
- 2.Alarm should sound with another frequency if motion is detected in PIR Sensor.

## **CIRCUIT LAYOUT:**

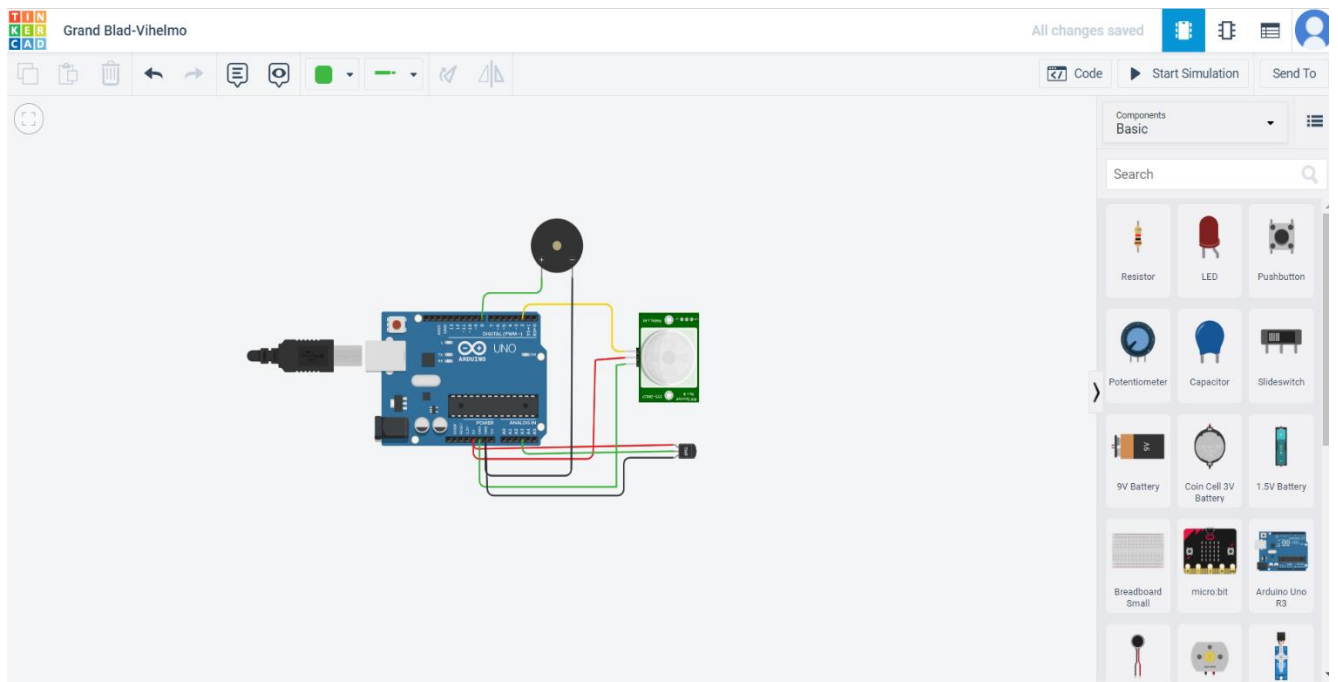


## CODE:

```
void setup()
{
  pinMode(A3, INPUT);
  pinMode(8, OUTPUT);
  pinMode(2, INPUT);
  Serial.begin(9600);
}
void loop()
{
  float temp;
  temp=analogRead(A3);
  temp=((temp*5)/1024);
  temp=(temp-0.5)*100;
  Serial.print("Temperature = ");
  Serial.print(temp);
  Serial.println(" C ");
  int motion=digitalRead(2);
  if (motion==1){
    Serial.println("Motion Detected");
    tone(8,15000);
    delay(3000);
  }
  else{
    Serial.println("No Motion");
    noTone(8);
  }
  if (temp<59)
    noTone(8);
  if (temp>=60)
    tone(8,1000);
    delay(5000);
}
```

**OUTPUT:**

**PASSIVE INFRARED SENSOR:**

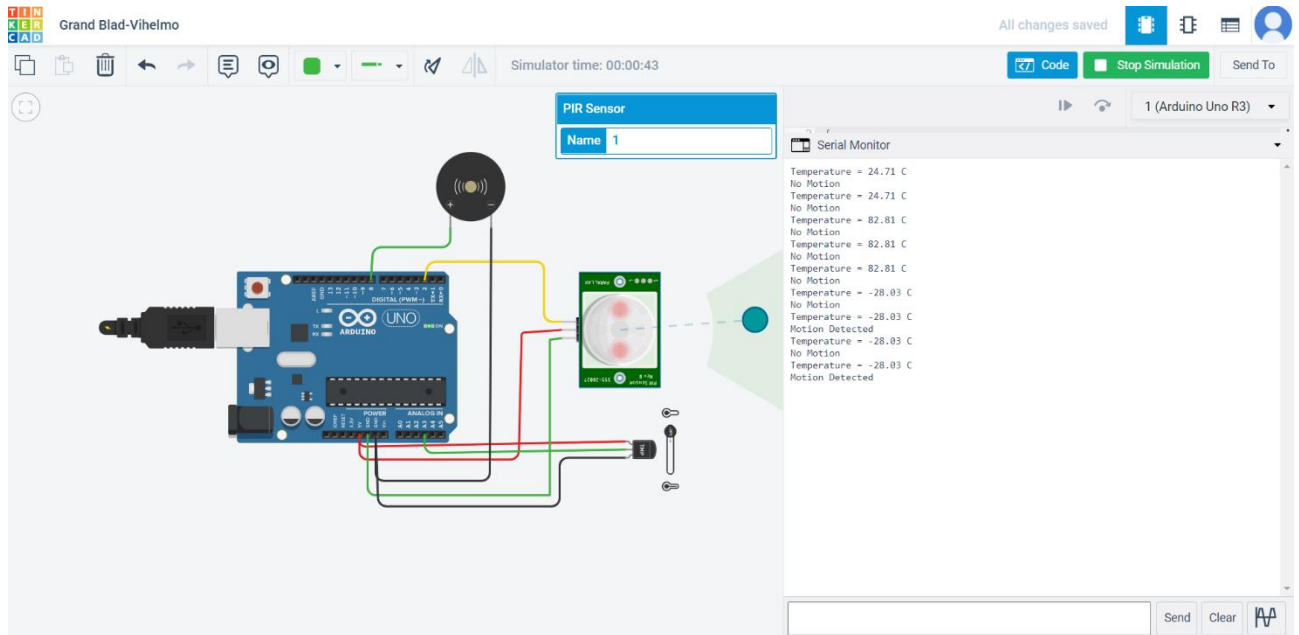

**TEMPERTURE SENSOR (AT 60°C):**

